
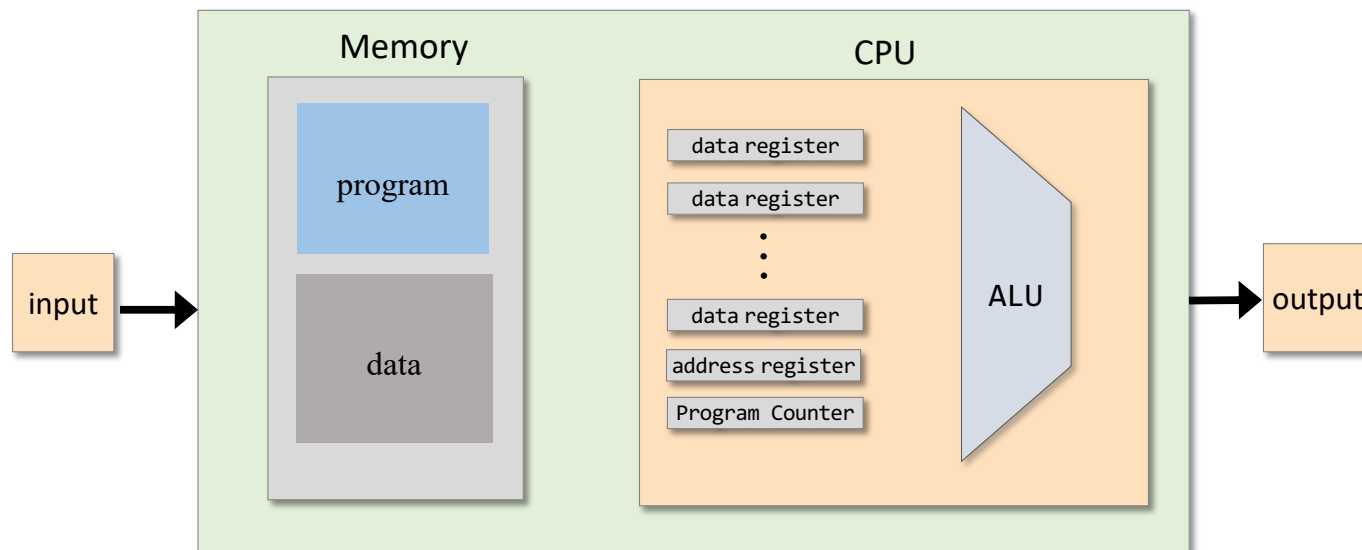


4. Architecture d'un ordinateur

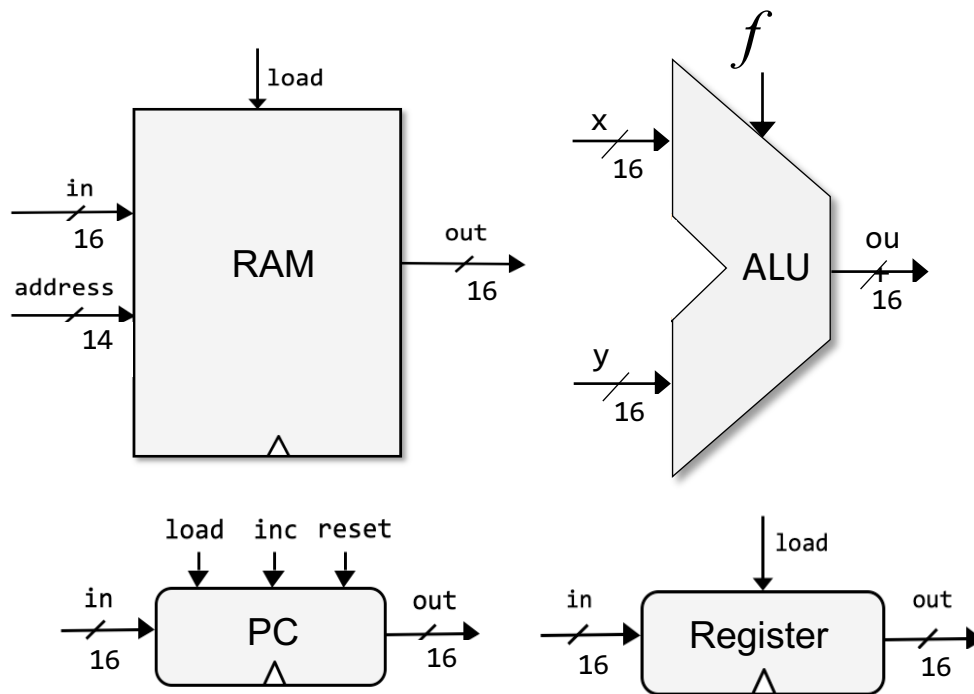

Les données du problème

Composants matériels




Langage machine


```
// Computes  $R1 = 1 + 2 + 3 + \dots + R0$ 
//  $i = 1$ 
@i
M=1
// sum = 0
@sum
M=0
(LLOOP)
// if ( $i > R0$ ) goto STOP
@i
D=M
@R0
D=D-M
@STOP
D;JGT
...
```

Construire une machine pour l'exécution d'un programme !


Architecture classique

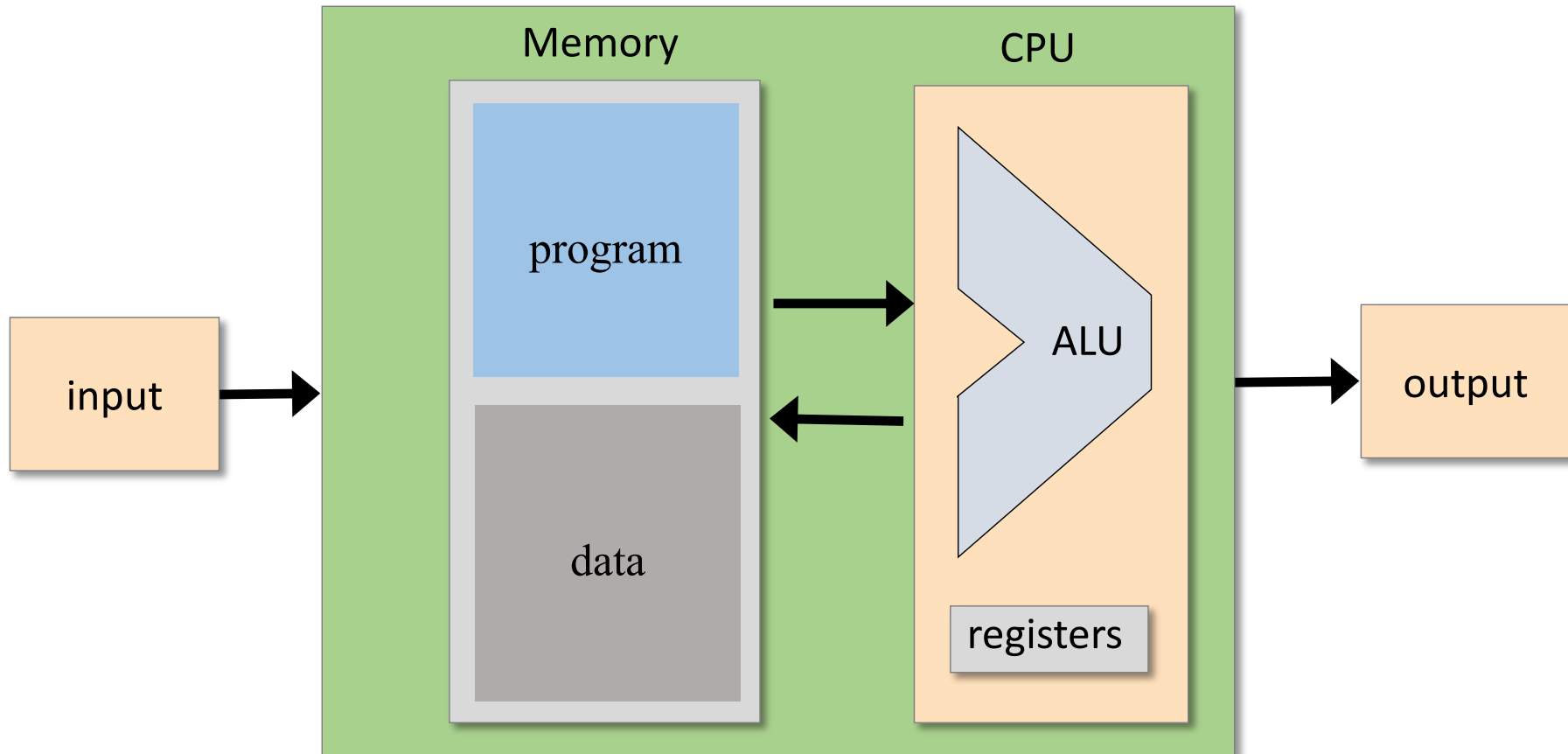

Architecture classique

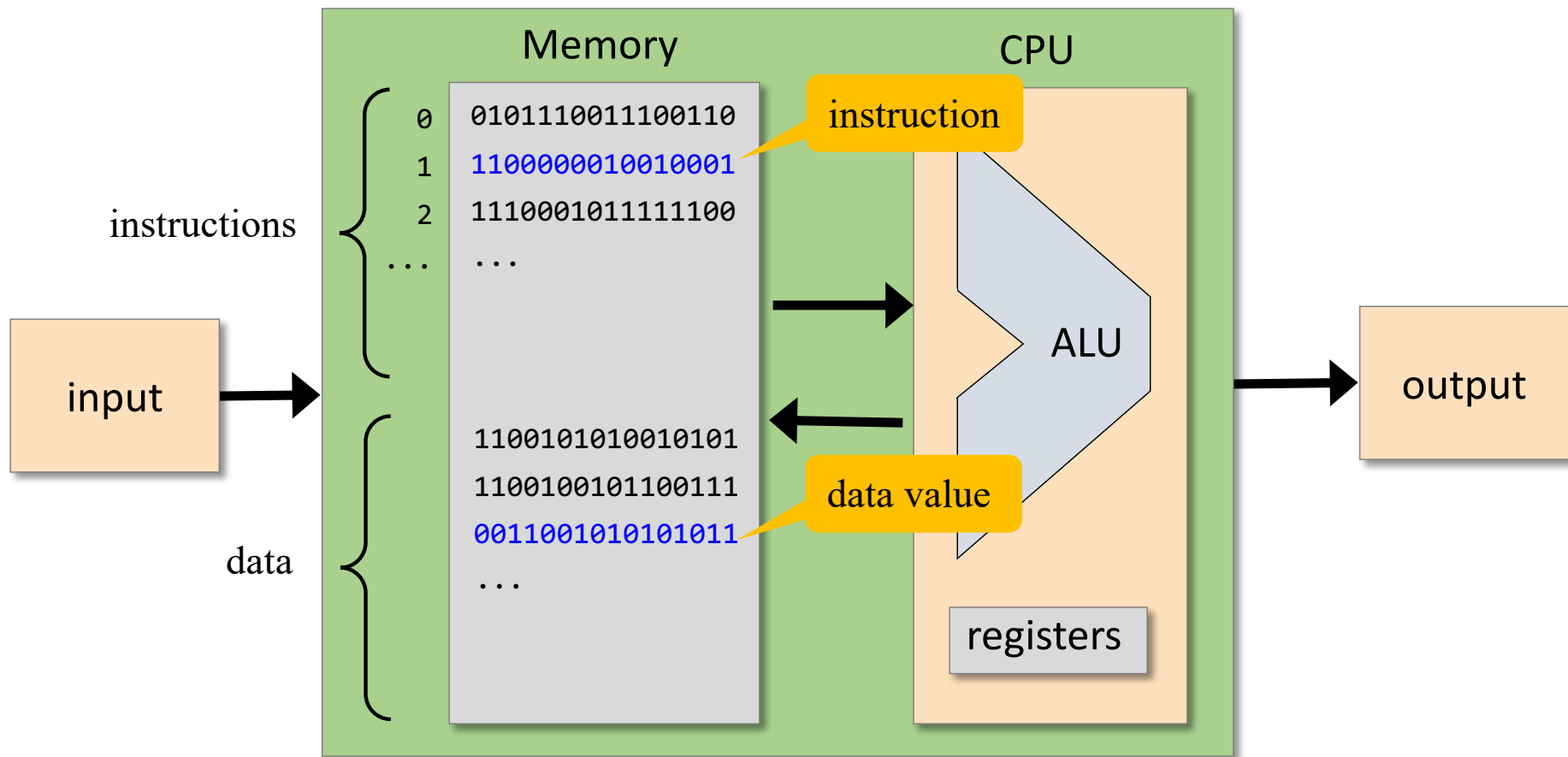

Implémentation de la Hack machine

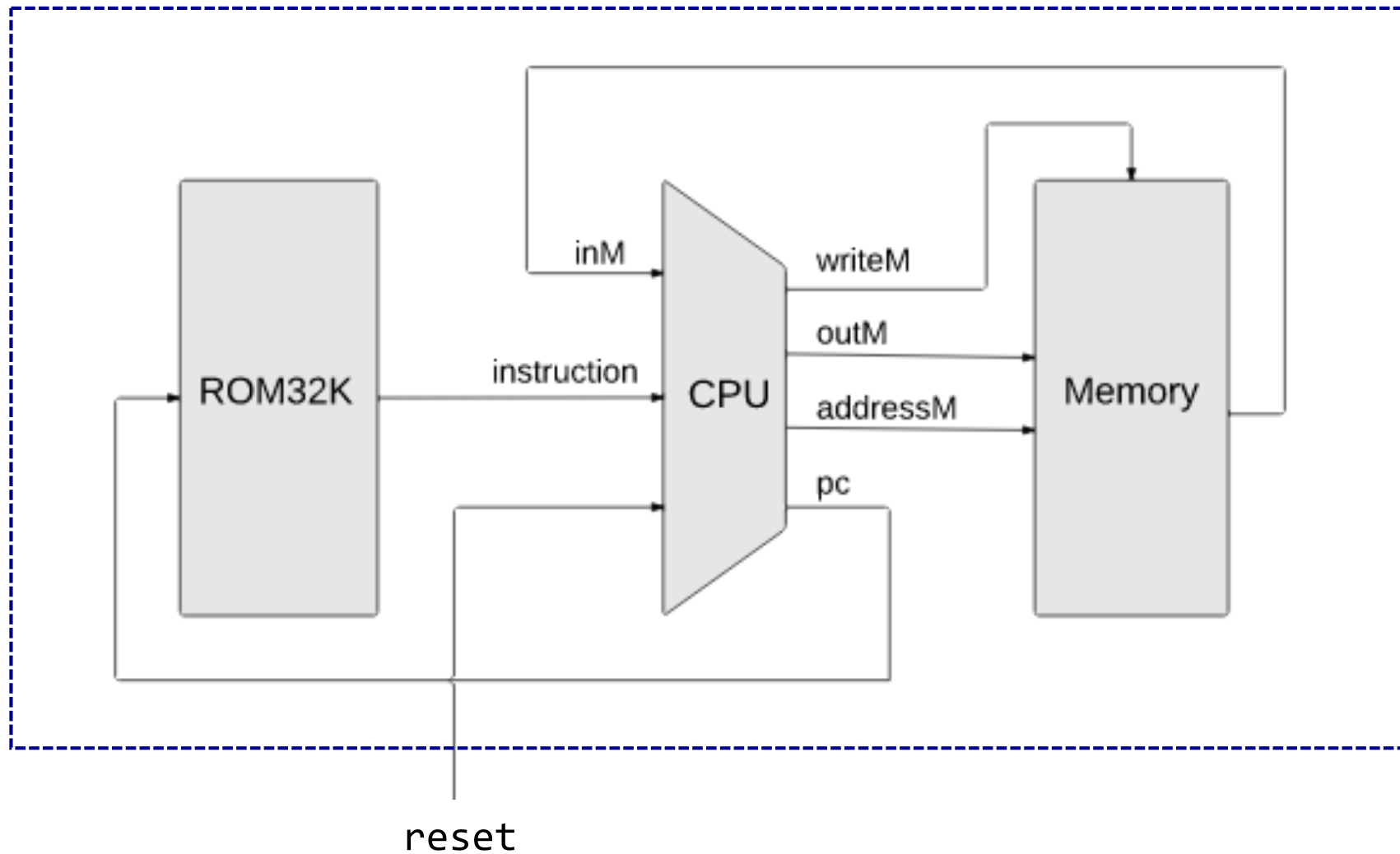

Hack language

A instruction

Symbolic: @xxx

(xxx is a decimal value ranging from 0 to 32767, or a symbol bound to such a decimal value)

Binary: 0 vvvvvvvvvvvvvvvvv (vv ... v = 15-bit value of xxx)

C instruction

Symbolic: dest = comp; jump

(comp is mandatory.

If dest is empty, the = is omitted;

If jump is empty, the ; is omitted)

Binary: 111acccccddjjj


		comp	c	c	c	c	c	c
0			1	0	1	0	1	0
1			1	1	1	1	1	1
-1			1	1	1	0	1	0
D			0	0	1	1	0	0
A	M		1	1	0	0	0	0
!D			0	0	1	1	0	1
!A	!M		1	1	0	0	0	1
-D			0	0	1	1	1	1
-A	-M		1	1	0	0	1	1
D+1			0	1	1	1	1	1
A+1	M+1		1	1	0	1	1	1
D-1			0	0	1	1	1	0
A-1	M-1		1	1	0	0	1	0
D+A	D+M		0	0	0	0	1	0
D-A	D-M		0	1	0	0	1	1
A-D	M-D		0	0	0	1	1	1
D&A	D&M		0	0	0	0	0	0
D A	D M		0	1	0	1	0	1

a == 0 a == 1

dest	d	d	d	Effect: store comp in:
null	0	0	0	the value is not stored
M	0	0	1	RAM[A]
D	0	1	0	D register (reg)
DM	0	1	1	RAM[A] and D reg
A	1	0	0	A reg
AM	1	0	1	A reg and RAM[A]
AD	1	1	0	A reg and D reg
ADM	1	1	1	A reg, D reg, and RAM[A]

jump	j	j	j	Effect:
null	0	0	0	no jump
JGT	0	0	1	if comp > 0 jump
JEQ	0	1	0	if comp = 0 jump
JGE	0	1	1	if comp ≥ 0 jump
JLT	1	0	0	if comp < 0 jump
JNE	1	0	1	if comp ≠ 0 jump
JLE	1	1	0	if comp ≤ 0 jump
JMP	1	1	1	unconditional jump

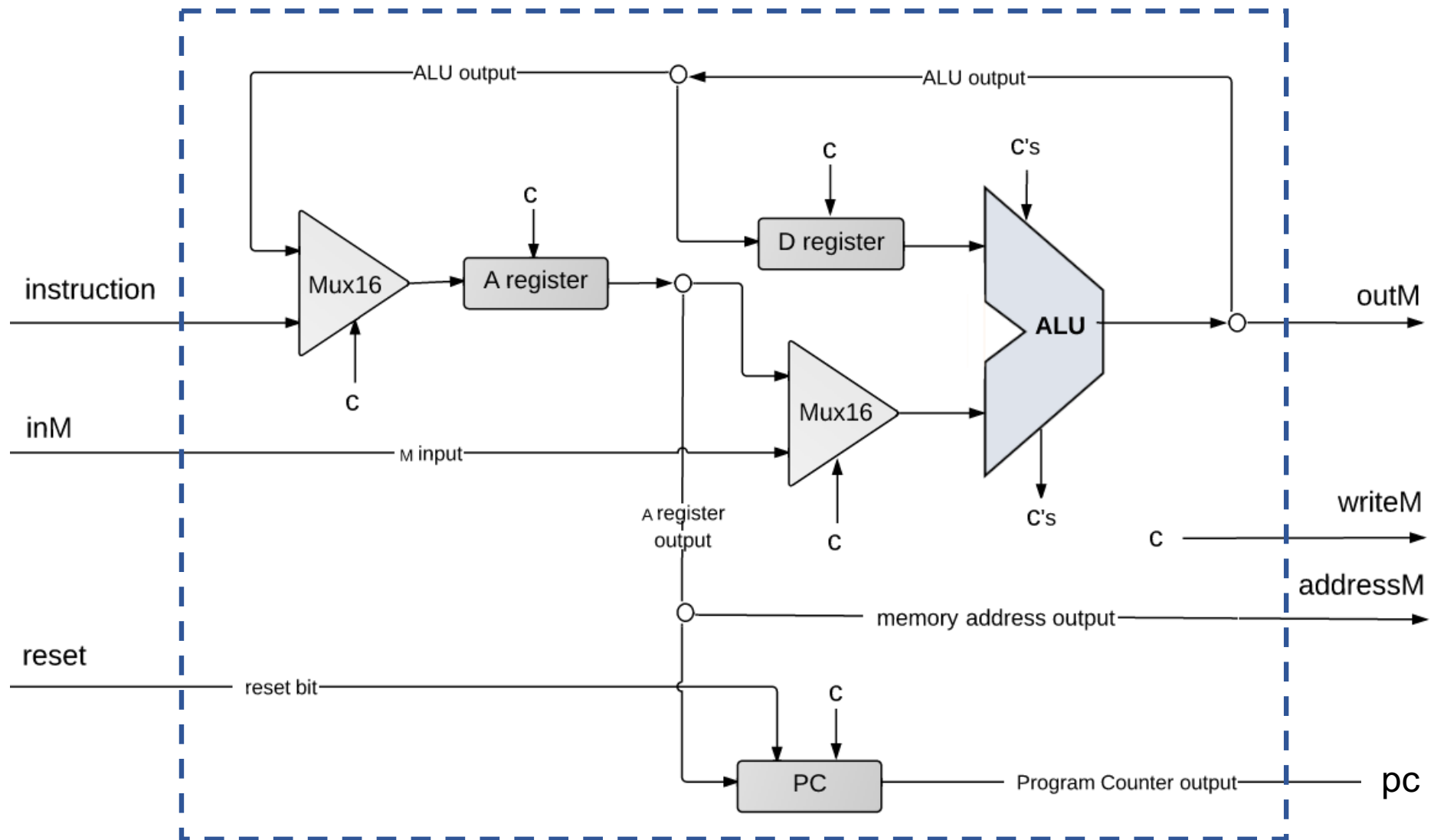Implémentation de la CPU de la Hack machine



Exercices : Calculer les fonctions de contrôles des Mux, registres et ALU.

HDL de la CPU

*/** Central Processing unit.*

Executes instructions written in Hack machine language.

CHIP CPU {

IN

inM[16], *// Value of M (RAM[A])*

instruction[16], *// Instruction to execute*

reset; *// Signals whether to execute the first instruction*
// (reset==1) or next instruction (reset == 0)

OUT

outM[16] *// Value to write to the selected RAM register*

writeM, *// Write to the RAM?*


addressM[15], *// Address of the selected RAM register*

pc[15]; *// Address of the next instruction*

PARTS:

// Put you code here:

}

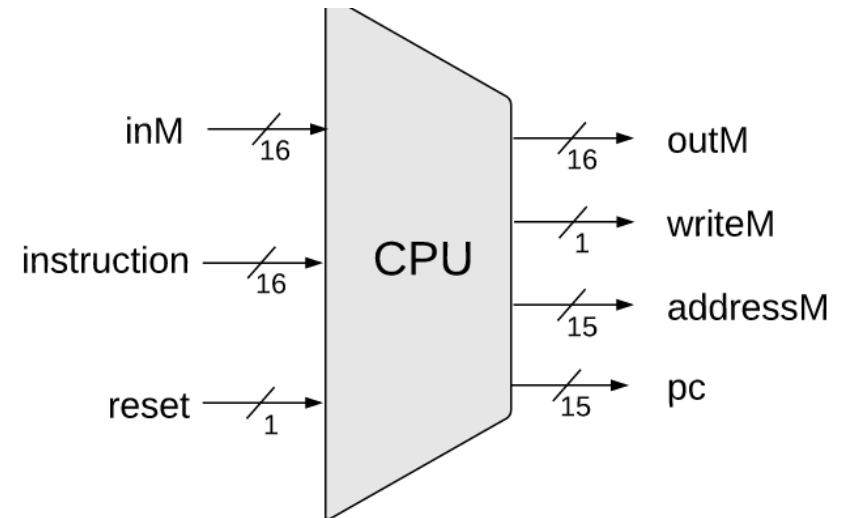

Questions